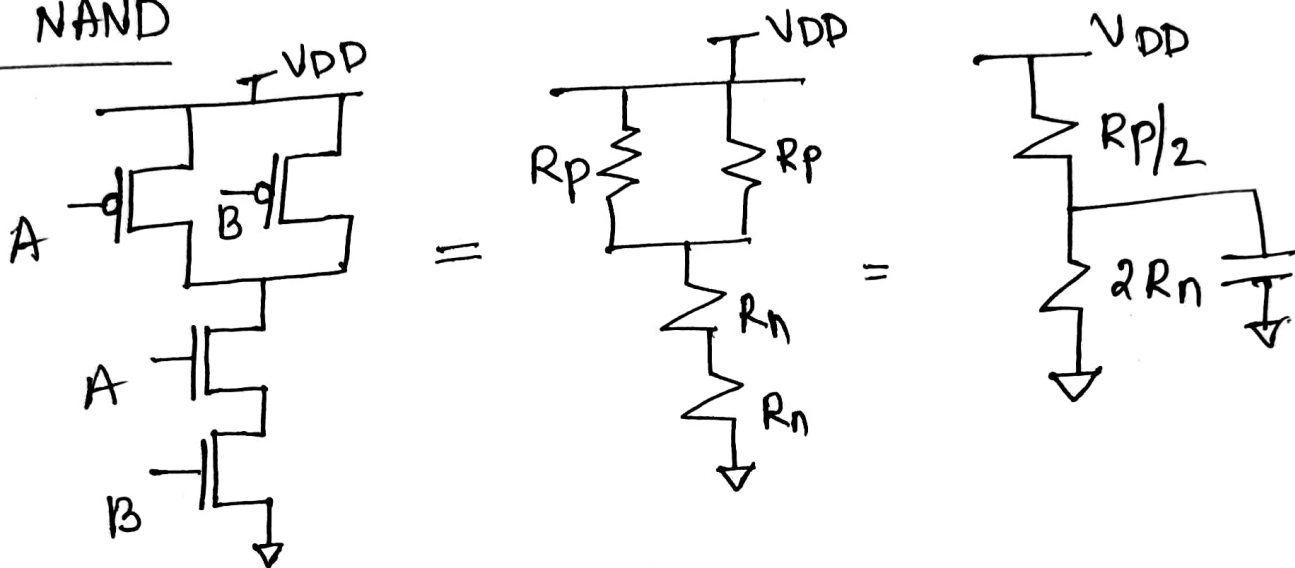


① Threshold voltage for CMOS inverter is

$$V_M = \frac{V_{DD} - |V_{tp}| + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

2-i/p NAND



$$\boxed{R_p \propto \frac{1}{\beta_p}} \quad \& \quad \boxed{R_n \propto \frac{1}{\beta_n}}$$

\therefore Threshold voltage for 2-i/p NAND gate is

$$V_M = \frac{V_{DD} - |V_{tp}| + V_{tn} \sqrt{\frac{\beta_n/2}{2\beta_p}}}{1 + \sqrt{\frac{\beta_n/2}{2\beta_p}}}$$

$$\Rightarrow V_M = \frac{V_{DD} - |V_{tp}| + \frac{1}{2} V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{2} \sqrt{\frac{\beta_n}{\beta_p}}}$$

For N-input NAND gate

$$V_M = \frac{V_{DD} - |V_{tp}| + \frac{V_{tn}}{N} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \frac{1}{N} \sqrt{\frac{\beta_n}{\beta_p}}}$$

we know that, $N \cdot M_L = V_{IL} - V_{OL}$, $V_{OH} = V_{DD}$
 $N \cdot M_H = V_{OH} - V_{IH}$, $V_{OL} = 0$

For CMOS Inverter:

$$V_{IH} = \frac{2V_{out} + V_{tn} + \frac{\beta_p}{\beta_n} (V_{DD} - |V_{tp}|)}{1 + \frac{\beta_p}{\beta_n}}$$

For 2-i/p NAND gate

$$V_{IH_N} = \frac{2V_{out} + V_{tn} + 4 \frac{\beta_p}{\beta_n} (V_{DD} - |V_{tp}|)}{1 + 4 \frac{\beta_p}{\beta_n}}$$

$\therefore R_p \rightarrow R_p/2$
 $R_n \rightarrow 2R_n$

For CMOS inverter


$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{tp}| + \frac{\beta_n}{\beta_p} V_{tn}}{1 + \frac{\beta_n}{\beta_p}}$$

For 2-i/p NAND gate β_p


$$V_{ILN} = \frac{2V_{out} - V_{DD} - |V_{tp}| + \frac{1}{4} \frac{\beta_n}{\beta_p} V_{tn}}{1 + \frac{1}{4} \frac{\beta_n}{\beta_p}}$$

② Given
$$F = \overline{A(D+E) + BC}$$

CMOS implementation is

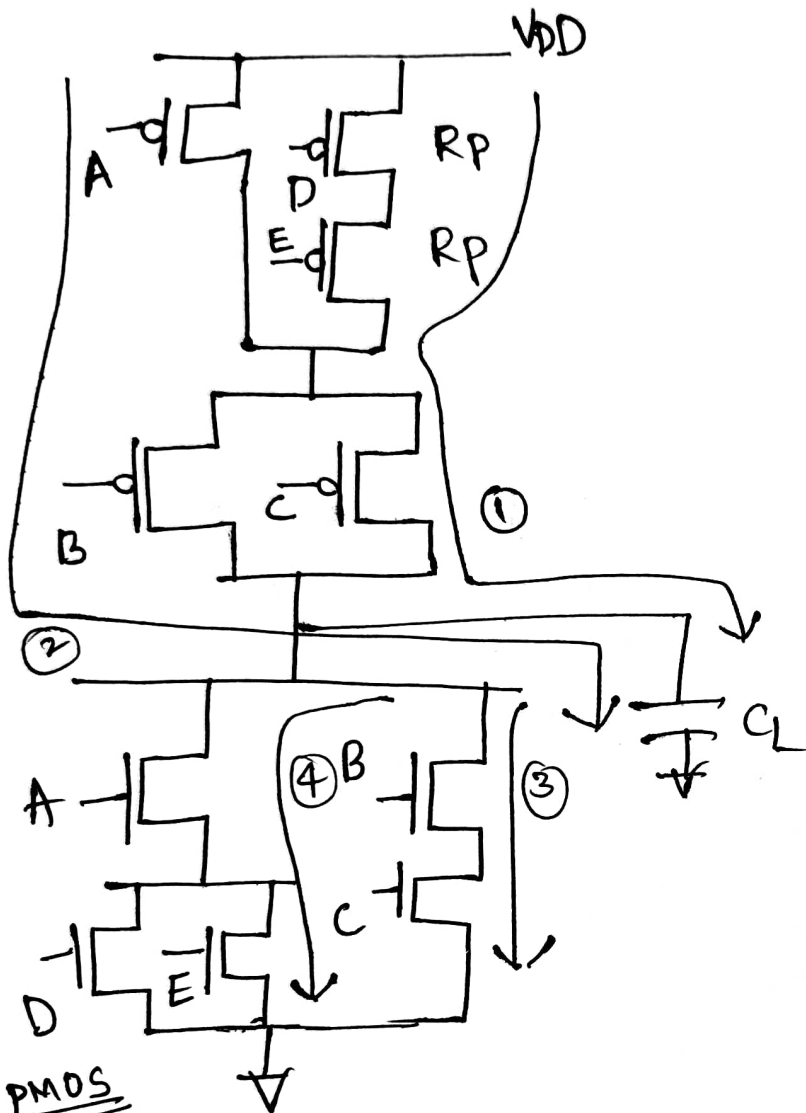

stand CMOS

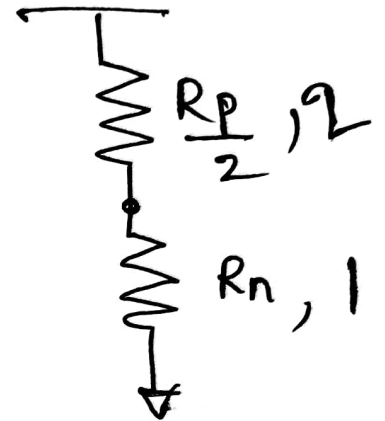

PMOS

① $\Rightarrow R_p + R_p + R_p \rightarrow \frac{R_p}{2} \Rightarrow 3R_p \rightarrow \frac{R_p}{2} \Rightarrow W = 6 \Rightarrow W_D = W_E = W_B = W_C = 6$

② $\Rightarrow x + \frac{R_p}{6} = \frac{R_p}{2} \Rightarrow x = \frac{R_p}{3} \Rightarrow W_A = 3$

NMOS


③ $\Rightarrow R_n + R_n \rightarrow R_n \Rightarrow 2R_n \rightarrow R_n \Rightarrow W = 2 \Rightarrow W_B = W_C = 2$

④ $\Rightarrow R_n + R_n \rightarrow R_n \Rightarrow 2R_n \rightarrow R_n \Rightarrow W = 2 \Rightarrow W_A = W_E = 2$
 $\Rightarrow W_D = 2$

③ Given $V_{DD} = 2V$, $C_{ox} = \frac{2fF}{\mu m^2}$, $C_{DBP} = 1fF$, $C_{DBN} = 0.5fF$

$$\left(\frac{W}{L}\right)_p = \frac{4}{0.5}, \quad k_p' = 100 \frac{\mu A^2}{V^2}, \quad |V_{tp}| = 0.5V$$
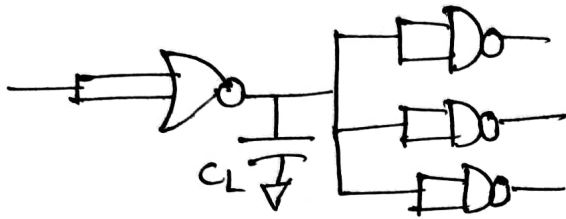
$$\left(\frac{W}{L}\right)_n = 2/0.5, \quad k_n' = 250 \frac{\mu A}{V^2}, \quad V_{tn} = 0.6V$$



a) $C_p = C_{DBP} + C_{DBN}$

$$C_p = 1fF + 0.5fF \Rightarrow C_p = 1.5fF$$

b) $C_{LC} = C_{g1} + C_{g2} + C_{g3} = 3C_{ox} = \frac{6fF}{\mu m^2}$

c) $C_L = C_p + C_{LC} = 1.5fF + \frac{6fF}{\mu m^2} = 7.5fF$

d) $R_p = \frac{2}{k_p' \left(\frac{W}{L}\right)_p (V_{DD} - |V_{tp}|)} = \frac{2}{100 \times 10^6 \times 2 \times (2 - 0.5)} = 0.833K\Omega$

e) $\tau = C_L R_p = 7.5 \times 10^{-15} \times 0.833 \times 10^3 = 6.24 \text{ ps} \times 2 = 12.48 \text{ ps}$

④ Given $\beta_n = 0.2 \frac{mA}{V^2}$, $\beta_p = 0.1 \frac{mA}{V^2}$, $V_{tn} = |V_{tp}| = 0.6$

$$V_{DD} = 3.3V$$

a) $V_M = \frac{V_{DD} - |V_{tp}| + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} = \frac{3.3 - 0.6 + 0.6 \sqrt{\frac{0.2}{0.1}}}{1 + \sqrt{\frac{0.2}{0.1}}}$

$$\Rightarrow V_M = \frac{3.548}{2.4142} \Rightarrow \boxed{V_M = 1.45V}$$

$$b) R_p = \frac{1}{\beta_p (V_{DD} - V_{tp})} = \frac{1}{0.1 \times 10^{-3} (3.3 - 0.6)} = 3.703 \text{ k}\Omega$$

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{tn})} = \frac{1}{0.2 \times 10^{-3} (3.3 - 0.6)} = 1.851 \text{ k}\Omega$$

$$c) t_r = 2.2 R_p C_p = 2.2 \times 3.703 \times 10^3 \times 9 \times 10^{-15} = 73.319 \text{ ps}$$

$$t_f = 2.2 R_n C_p = 2.2 \times 1.851 \times 10^3 \times 9 \times 10^{-15} = 36.649 \text{ ps}$$

$$d) t_r = 2.2 R_p (C_p + C_L) = 2.2 \times 3.703 \times 10^3 \times 34 \times 10^{-15} = 276.984 \text{ ps}$$


$$t_f = 2.2 R_n (C_p + C_L) = 2.2 \times 1.851 \times 10^3 \times 34 \times 10^{-15} = 138.4548 \text{ ps}$$

$$e) t_{HL} = 0.693 R_p (C_p + C_L) = 0.693 \times 3.703 \times 10^3 (9 + 25) \times 10^{-15} = 87.179 \text{ ps}$$

$$t_{LH} = 0.693 R_n (C_p + C_L) = 0.693 \times 1.851 \times 10^3 (9 + 25) \times 10^{-15} = 43.589 \text{ ps}$$

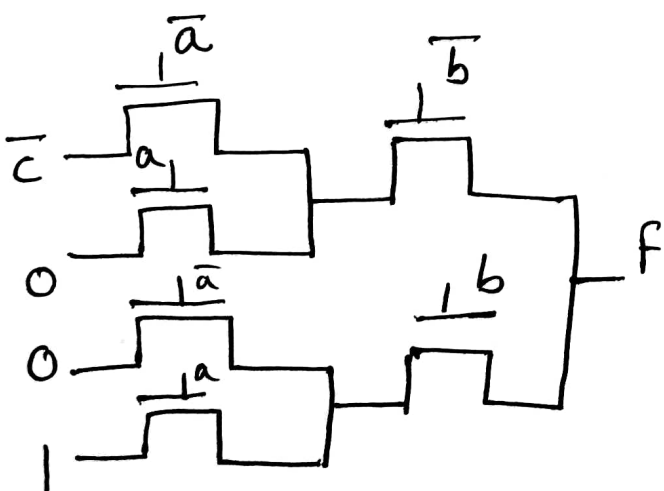
8) b)

$$f(a, b, c) = ab + \bar{a} \bar{b} \bar{c}$$




a	b	f
0	0	0
0	1	0
1	0	0
1	1	1

8)

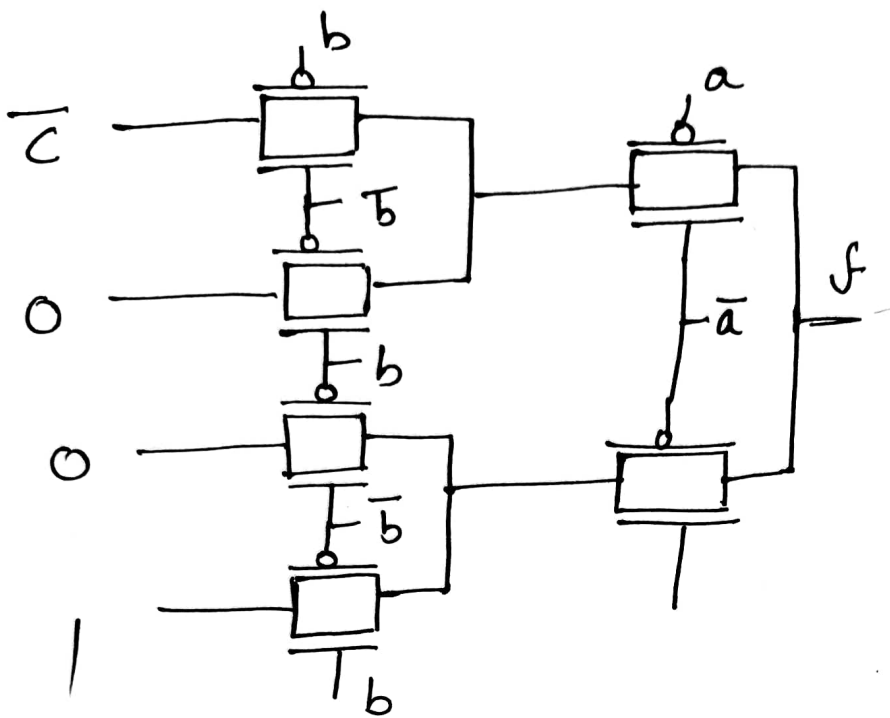

9)

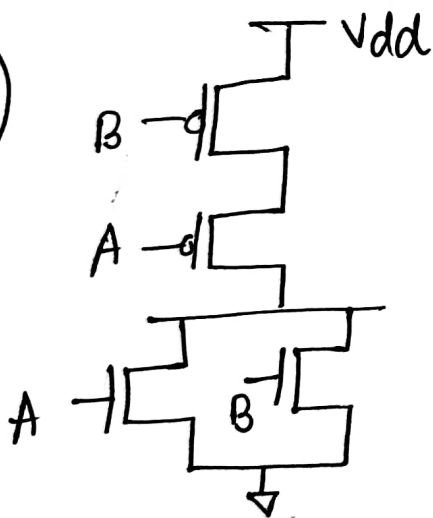

case (i) $A, B \rightarrow$ long time zero & $B \rightarrow 0 \text{ to } V_{DD}$

$$\text{Then } R_{\text{peq}} = 2R_p$$

$$R_{\text{neq}} = R_n$$

$$\Rightarrow t_{LH} = 0.693(2R_p)C \text{ and } t_{HL} = 0.693(R_n)C \rightarrow (1)$$

case (ii) $A, B \rightarrow$ long time zero & $A, B \rightarrow 0 \text{ to } V_{DD}$



$$\Rightarrow R_{\text{peq}} = 2R_p \text{ \& } R_{\text{neq}} = \frac{R_n}{2}$$

$$t_{LH} = 0.693(2R_p)C \text{ \& } t_{HL} = 0.693\left(\frac{R_n}{2}\right)C \rightarrow (2) \text{ From (1) \& (2)}$$

$$t_{pd1} > t_{pd2}$$

\therefore case (i) have more delay

10) Given circuit

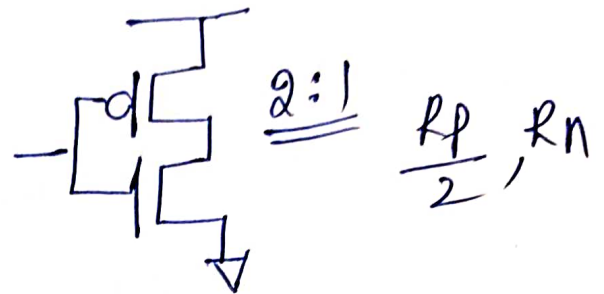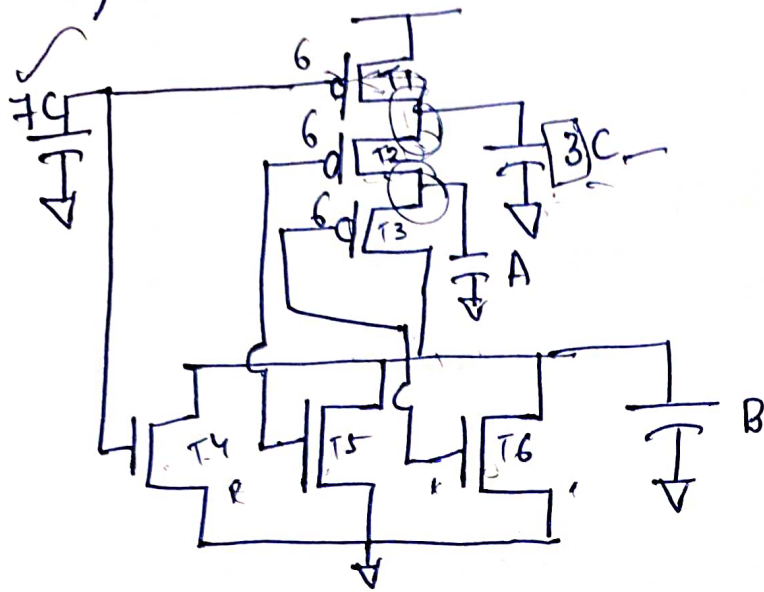

Here $B = C_{d3} + C_{d4} + C_{d5} + C_{d6}$, $A = 6C$
 $= 6C + C + C + C$
 $B = 9C$


ii) a) If $D=0$ then $\overline{OUT} = ((AB)(E+F)) + CG$

If $D=1$ then $\overline{OUT} = (AB+C) \cdot (E+F+G)$

Final Expression is

$$OUT = \overline{D} [(AB) \cdot (E+F) + CG] + D [(AB+C) \cdot (E+F+G)]$$

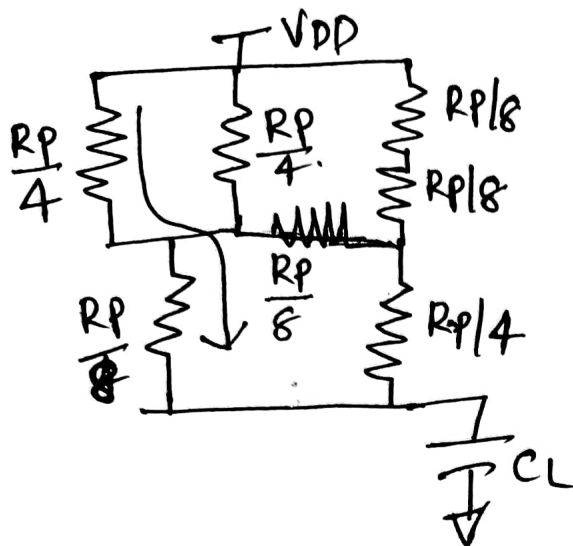ii) b PULL UP NETWORK (equivalent circuit is)



Here the worst case resistance is $\frac{1}{8}$
 input pattern, \therefore initial $E=F=G=D=0, A=B=C=1$ (this is one possibility)


$$R_{P_{eq}} = \frac{R_P}{8} + \frac{R_P}{8} + \frac{R_P}{8} + \frac{R_P}{4} = \frac{R_P + R_P + R_P + 2R_P}{8} = \frac{5R_P}{8}$$

or

$$R_{P_{eq}} = \frac{R_P}{4} + \frac{R_P}{8} + \frac{R_P}{4} = \frac{2R_P + R_P + 2R_P}{8} = \frac{5R_P}{8}$$

Input pattern:-

PULL DOWN NETWORK (equivalent circuit)

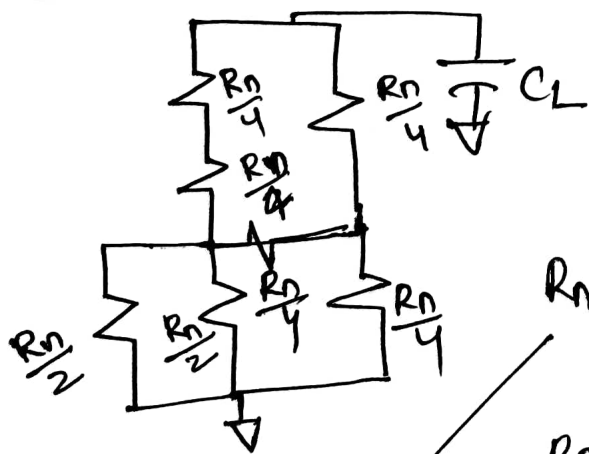

Here the worst case resistance is




$$R_{n_{eq}} = \frac{R_n}{4} + \frac{R_n}{4} + \frac{R_n}{4} + \frac{R_n}{4} = R_n$$

or

$$R_{n_{eq}} = \frac{R_n}{4} + \frac{R_n}{4} + \frac{R_n}{2} = R_n$$

input pattern (final) :- $A=B=D=G=1$ (this is one possibility)
 $C=E=F=0$

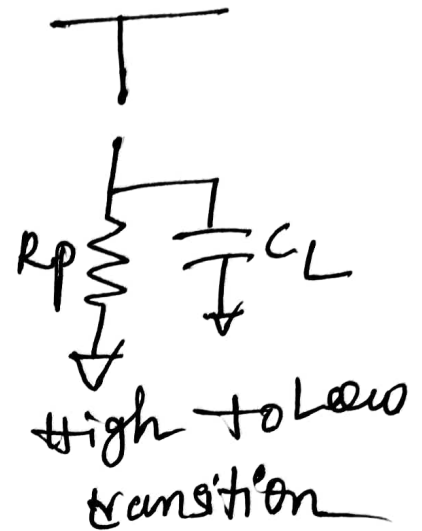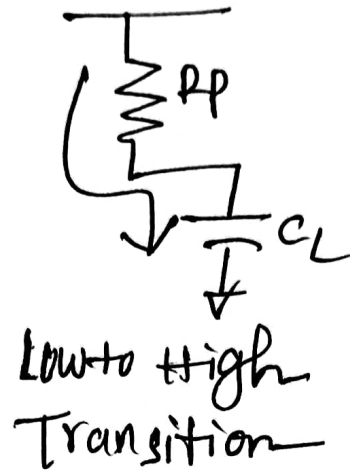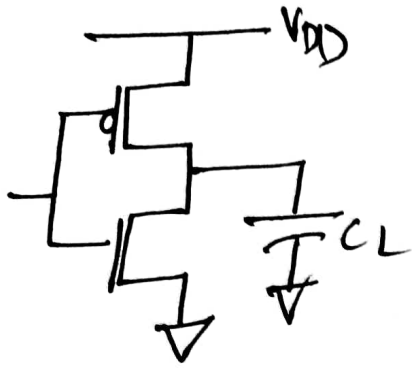5) Dynamic power dissipation of CMOS inverter



During transition of the output from low to high, the energy drawn from the supply

$$\begin{aligned}
 E_{0 \rightarrow 1} &= \int_0^{V_{DD}} P(t) dt = \int_0^{V_{DD}} V_{DD} i(t) dt \\
 &= \int_0^{V_{DD}} V_{DD} C_L \frac{dV_O}{dt} dt \\
 &= V_{DD} C_L \int_0^{V_{DD}} dV_O \\
 &= V_{DD} C_L \times [V_{DD} - 0]
 \end{aligned}$$

$$\boxed{E_{0 \rightarrow 1} = V_{DD}^2 C_L} \rightarrow \textcircled{1}$$

The Energy stored in the capacitor is

$$E_C = \int_0^{V_{DD}} V_O \times C_L \frac{dV_O}{dt} dt$$

$$\Rightarrow E_c = C_L \times \left[\frac{V_0^2}{2} \right]_0^{V_{dd}}$$

$$\Rightarrow \boxed{E_c = \frac{C_L V_{dd}^2}{2}} \rightarrow (2)$$

From ① & ② I can say that, out of total energy drawn from supply ($V_{dd}^2 C_L$), half of the energy stored in C_L and remaining half is dissipated in PMOS network and remaining $\frac{1}{2} C_L V_{dd}^2$ (stored in C_L) is dissipated through NMOS transistor.

$$\begin{aligned} E_{dis} &= \int_0^0 V_c(t) i(t) dt \\ &= \int_{V_{dd}}^0 V_c(t) \times -C_L \frac{dV_c(t)}{dt} dt \\ &= -C_L \left[\frac{V_c^2}{2} \right]_{V_{dd}}^0 \end{aligned}$$

$$\boxed{E_{dis} = \frac{1}{2} C_L V_{DD}^2}$$

Now dynamic power dissipation

$$\begin{aligned} P_d &= E_c \times f \Rightarrow P_d = \frac{1}{2} \frac{C_L V_{dd}^2}{T} \\ &\Rightarrow P_d = \frac{1}{2} C_L V_{dd}^2 f \end{aligned}$$

$$\Rightarrow \boxed{P_d = \frac{1}{2} \alpha_{0 \rightarrow 1} C_L V_{dd}^2 f}$$